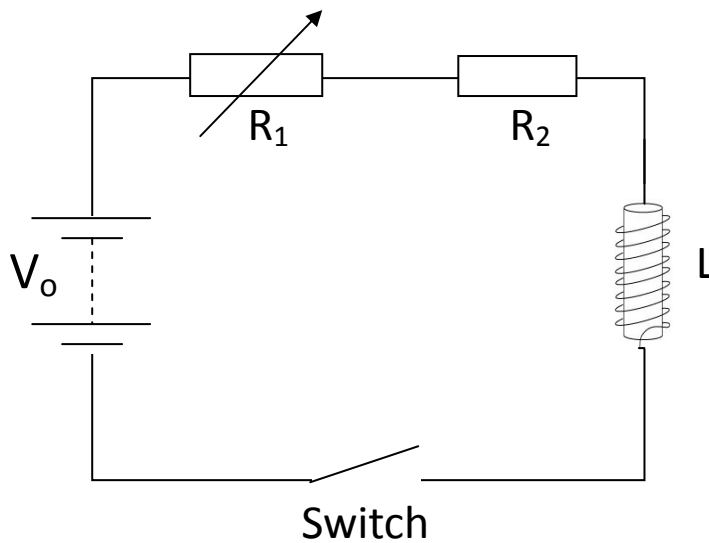


Growth of current in an RL d.c. circuit



In the above circuit, the two resistors obey Ohm's law, i.e.

$$V = IR.$$

The inductor L is assumed to have no resistance, it will generate a back emf whenever there is a change in the current passing through it,

$$\epsilon = -L \frac{dI}{dt}$$

Around the circuit, total emf = total p.d. Hence,

$$V_0 + \epsilon = I(R_1 + R_2) \quad \text{or}$$

$$V_0 - L \frac{dI}{dt} = I(R_1 + R_2) \quad \dots\dots\dots(1)$$


Eq (1) leads us to the solution of the current as a function of time t .

With the initial condition $I = 0$ at $t = 0$, Eq (1) is solved

$$I = \frac{V_0}{R} \left(1 - e^{-\frac{t}{\tau}}\right) \dots\dots\dots(2)$$

Where $R = R_1 + R_2$ is the total resistance and $\tau = \frac{L}{R}$ is called the time constant of the LR circuit.

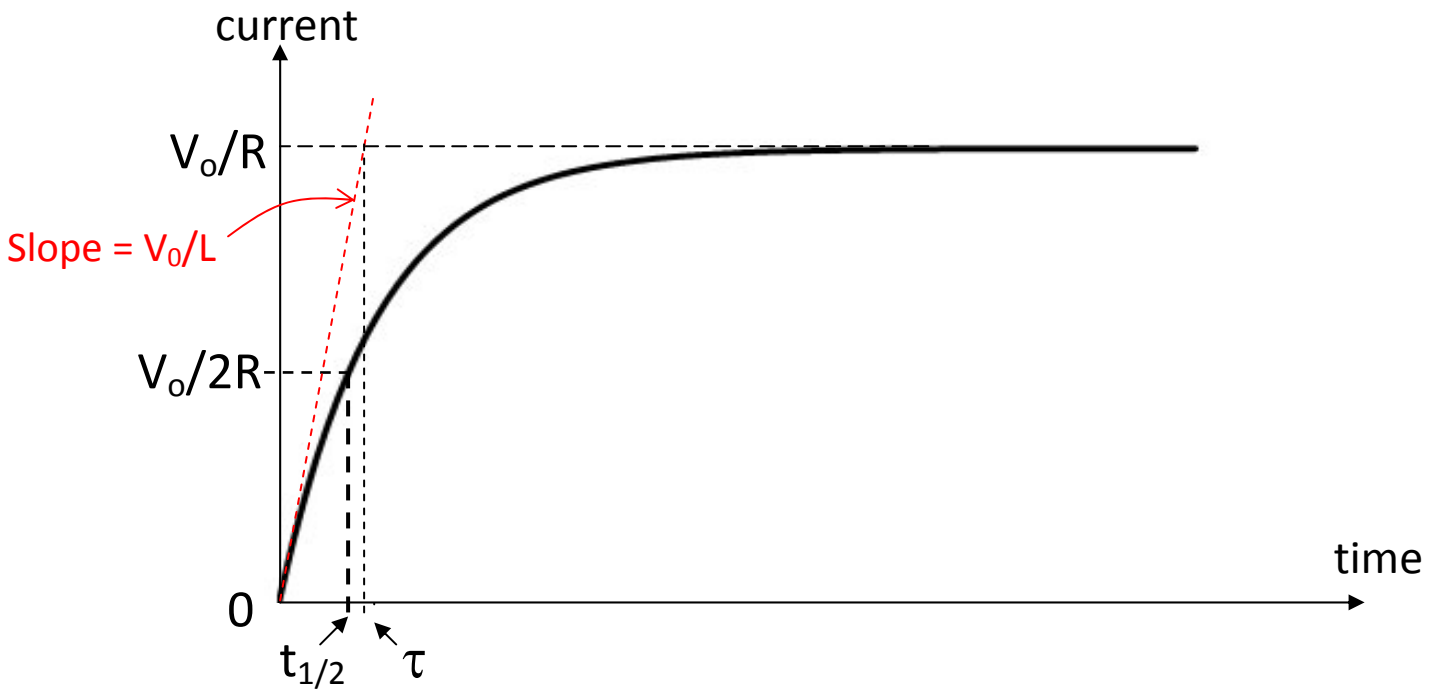According to Eq (2), we get the graph of I-t.



- The current **rises exponentially** and eventually up to the steady value V_0/R . Inductance L can be regarded as a kind of inertia, it hinders any changes of current in the circuit.


- Putting $I = 0$ (the current at $t = 0$) in Eq (1), we obtain the initial rate of rise of current, $di/dt = V_0/L$. Thus, the red dotted line shown in the above graph has the slope V_0/L .

- The time $t_{1/2}$ is the half-life, it is the time for the current rising to half of its steady value V_0/R .

Mathematically,


$$t_{1/2} = \tau \ln 2 = \frac{L}{R} \ln 2$$

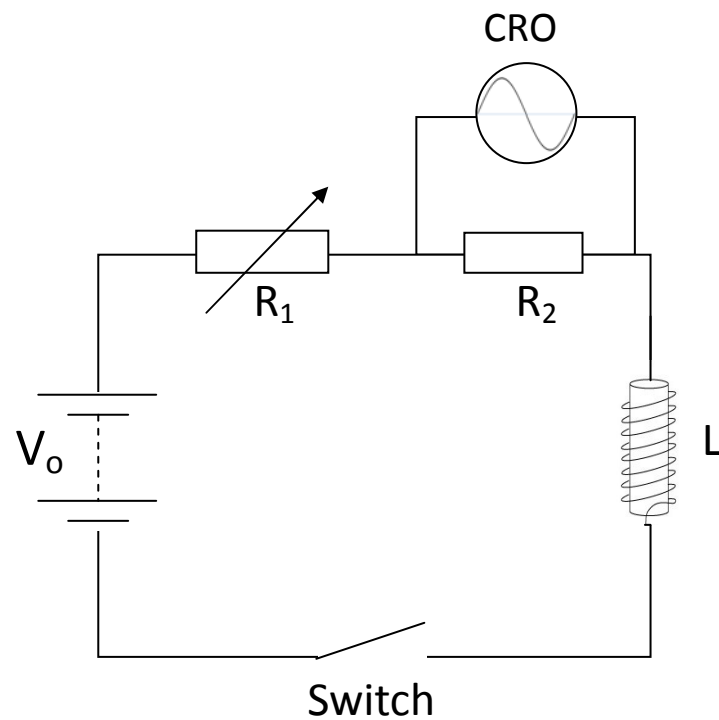- The time constant τ (or half life $t_{1/2}$) gives us a sense on how long the transient stage is about to last. If $L = 0$, the current will build up to the steady value immediately after the switch is closed.
- As a CRO is used to monitor the time-varying current, we can connect it in this way:



The trace displayed on the CRO is therefore the voltage across R_2 . Nevertheless, the trace is absolutely identical to the current-time graph, except that the final steady value is now replaced by $V_0 \left(\frac{R_2}{R_1 + R_2} \right)$. The exponential curve, the time constant and the half-life are all the same.

Example

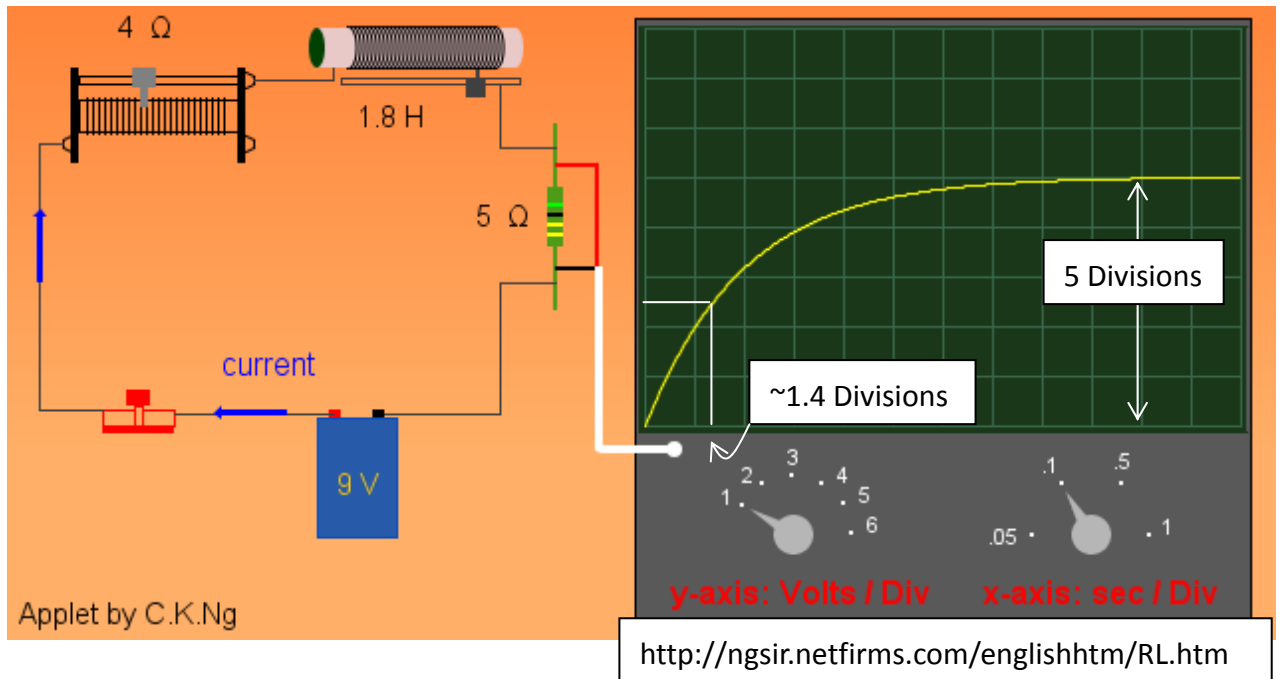

Calculations:

1. On the CRO, Steady value = 5 Divisions, which corresponds to $5 \text{ Div} \times 1 \text{ V/Div} = 5\text{V}$.

Theoretically, the voltage of battery 9V is finally divided between the 4Ω and the 5Ω resistors. The part shared by the 5Ω resistor is $9 \times 5 / (5+4) = 5\text{V}$.

2. On the CRO, the half-life is observed to be $\sim 1.4 \text{ Div}$. It corresponds to $1.4 \text{ Div} \times 0.1\text{sec/Div} = 0.14\text{s}$.

Theoretically, $t_{1/2} = \tau \ln 2 = \frac{L}{R} \ln 2 = \frac{1.8}{4+5} \ln 2 = 0.138\text{s}$.